

SECTION - A

There are **FOUR** questions in this section. Answer **Question No. 1** and any **TWO** from the rest.

1. Write short notes (any two) from the following: (15×2=30)
 - (a) Buddhist Torana
 - (b) Ladh Khan Temple at Ahole
 - (c) Free standing Monoliths at Mahabalipuram
2. (a) Identify the different parts of the Stupa through required illustrations. (8)
 (b) Illustrate the development of the Chaitya halls with necessary sketches. (12)
3. (a) Compare between Gopuram and Vimana. (8)
 (b) Use necessary sketches to interpret the following statement-‘The temple becomes the fort and the fort becomes the city’ (12)
4. (a) Describe the different elements of a typical. Indo-Aryan temple. Use necessary examples and sketches. (10)
 (b) Discuss how the apsidal ended Buddhist Chaityahall was adopted for hindu temple formation. (10)

SECTION - B

There are **FOUR** questions in this Section. Answer **Question No. 5** and any **TWO** from the rest.

5. (a) Compare the architectural features of ‘Tomb Architecture’ between the ‘Slave Dynasty’ and the ‘Mughal Period’. (15)
 (b) Categories the architectural design strategies embedded in the architecture of ‘Jahangiri Mahal’ within the Agra Fort Premise. (15)
6. How is the architecture of ‘Houz Khas’ novel in terms of functional arrangements, spatial articulation and building volume? (20)
7. Explain the influences behind the development of ‘Fatehpur Sikri’ master plan and its architecture in terms of political and socio-cultural practice. (20)
8. Write short notes on the following topics: (10×2=20)
 - (a) Qutub Minar
 - (b) Chahar Bagh Gardens

Sub: **EEE 373** (Electrical and Electronic Installation for Buildings)

Full Marks: 140

Time: 3 Hours

The figures in the margin indicate full marks.

The corresponding Course Outcomes (COs) of each part of Question 1 and 5 are mentioned on the right most column. The COs of the Course are mentioned at the end of the question paper.

USE SEPARATE SCRIPTS FOR EACH SECTION

SECTION – AThere are **FOUR** questions in this section. Answer to **Question No. 1** is **compulsory**.Answer any **TWO** questions from Questions 2-4.

1. (a) Voltage across and current through a load are respectively $5\sin(100t + 30^\circ)$ and $1.5\cos(100t - 20^\circ)$. Between voltage and current which one is leading and at what angle? Find the value of circuit elements (R, L or C) that comprise the load. [Use phasor approach]

(8)
(CO2)

- (b) Consider a reading room of $20\text{m} \times 16\text{m}$ which needs an illuminance of 300 lux. How many bulbs of 1250 lumen need to have desired illuminance? How many fans need to be installed in this room?

(4½)
(CO1)

- (c) Using source transformation principle determine the value of V_x shown in the circuit, Fig. for Q 1(c).

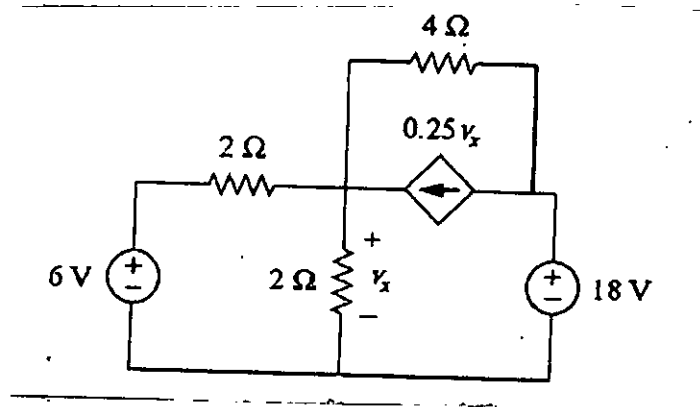
(11)
(CO1)

Fig. for Q 1(c)

EEE 373

2. (a) Using superposition theorem, find the expression of V_0 shown in the circuit, Fig. for Q 2(a). (12)

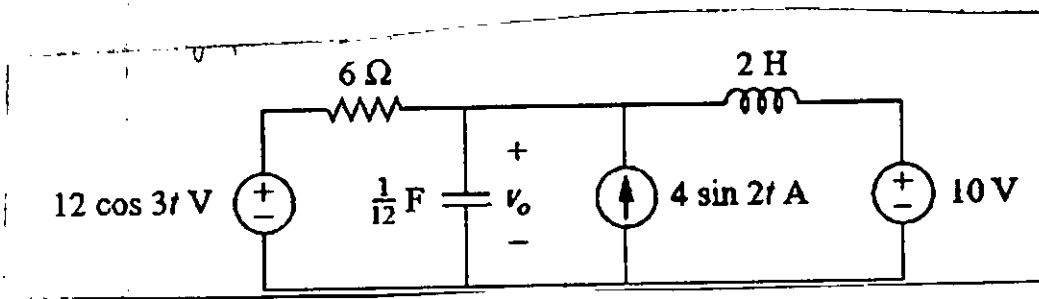


Fig. for Q 2(a)

- (b) In the circuit, Fig. for Q 2(b) Norton equivalent impedance as seen from terminal a-b. ($\frac{1}{3}$)

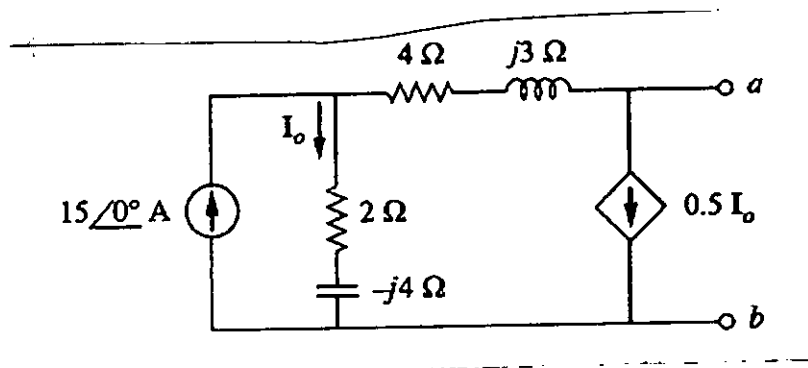


Fig. for Q 2(b)

3. (a) In the circuit Fig. for Q 3(a), R_L is adjusted until it absorbs maximum power. Find the value of R_L and the maximum power it absorbs. (12)

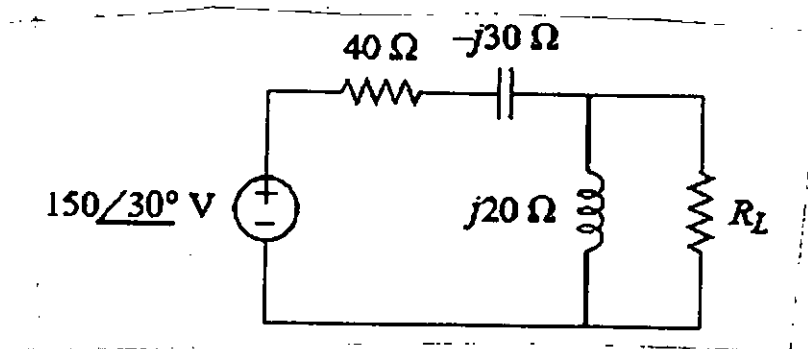


Fig. for Q 3(a)

- (b) Determine the power factor of the entire circuit shown in figure 3(b). Also determine the reactive power delivered by the source. (11 $\frac{1}{3}$)

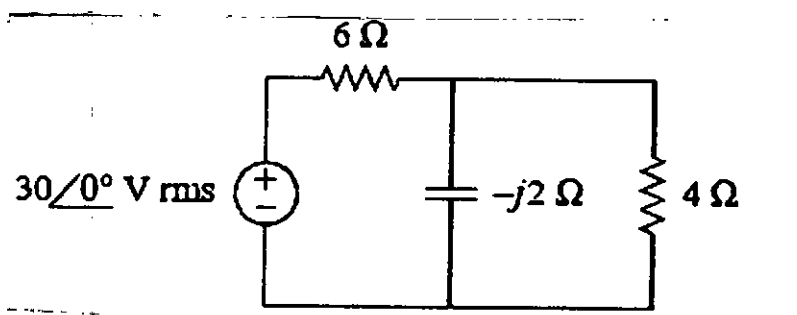


Fig. for Q. 3(b)

EEE 373

4. (a)

(16)

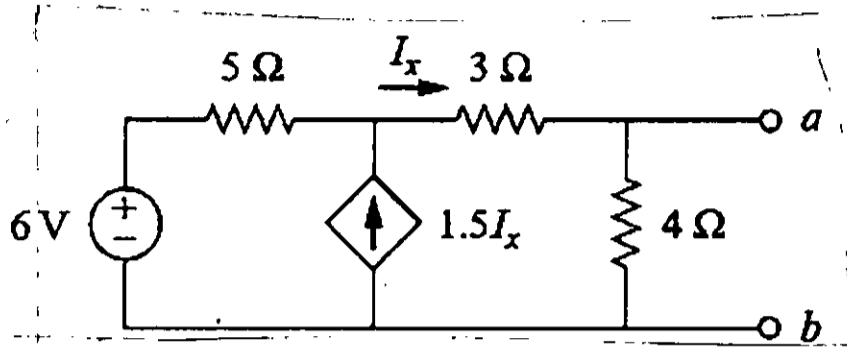


Fig. for Q 4(a)

- (i) Determine the Thevenin equivalent circuit of the Fig. for Q 4(a) to the left of the terminals a-b.
- (ii) Using source transformation, find the Norton equivalent circuit.
- (iii) A variable load is connected between terminals a-b. Draw a typical curve of the load power vs. load resistance. Also determine the peak point in this curve.

(b) A parallel RLC circuit has following node equation

(7 1/3)

$$\frac{dv}{dt} + 50v + 100 \int v dt = 110 \cos(377t - 10^\circ)$$

Find v(t) using phasor approach.

SECTION - B

There are **FOUR** questions in this section. Answer to **Question No. 5** is compulsory.

Answer any TWO questions from Questions 6-8.

5. Fig. for Q5 (i) shown a fitting and fixture layout, and Fig for Q5 (ii) current rating for different types of copper cables. In the diagram, each fan has rated power of 250 W at 220 Vac, each light has rated power of 40 W and each of the sockets have rated power of 3500 W.

(12 + 6 + 6)
(CO3)

- (a) Design an appropriate conduit layout, clearly indicating the cable ratings for each line, satisfying power requirement. Write justification for choosing a particular cable.
- (b) Draw Switch Board Connection Diagram for each room
- (c) Draw the Distribution Board Connection Diagram

Contd P/4

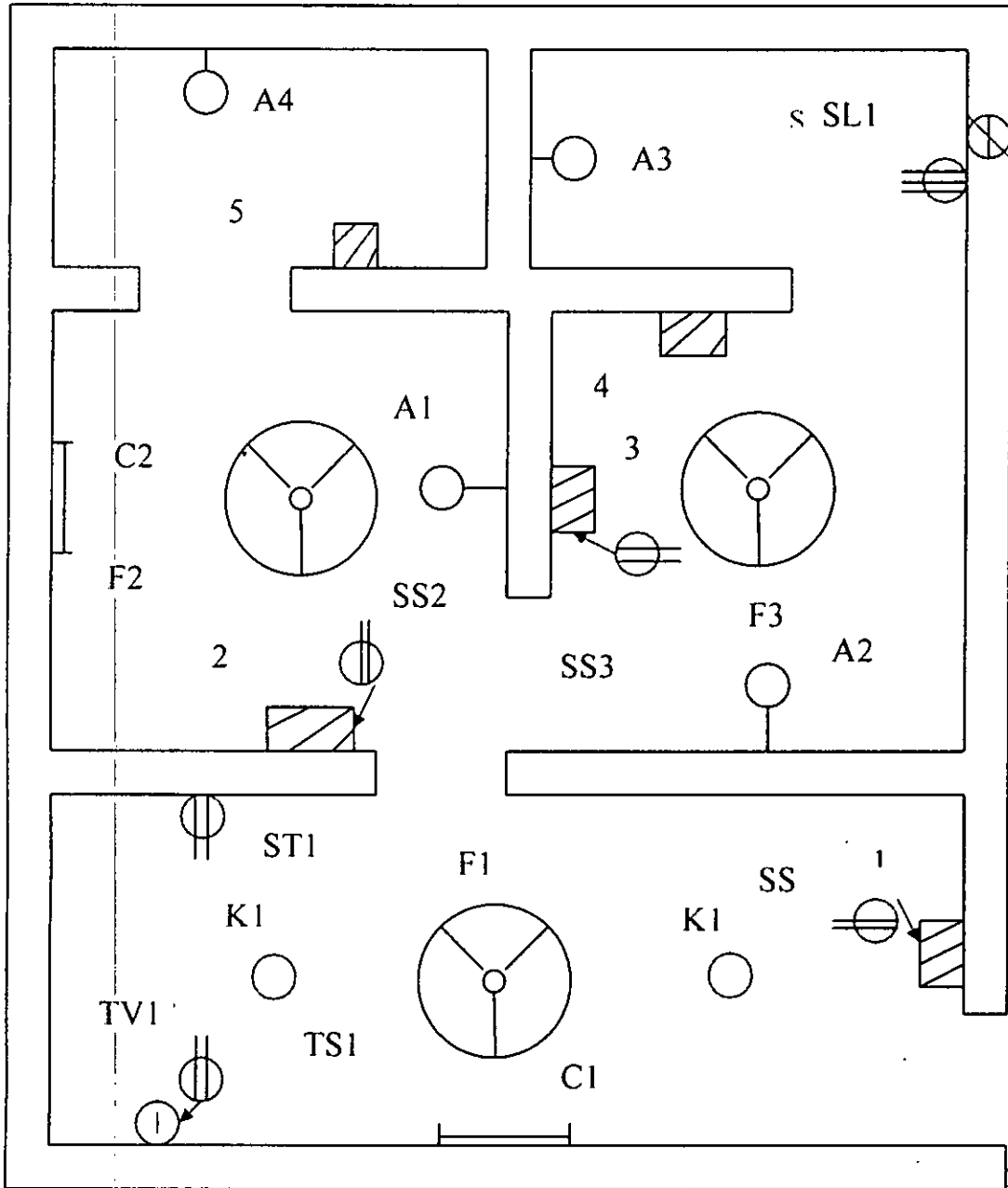


Fig for Q 5 (i)


Cable Rating Table

Cross Sectional Area	No. & Approx. Diameter of wire Cu/Al	Nominal Thickness of Insulation	Current rating at 30°C in ground	
			Copper 125 amps	Aluminium amps
Core x mm ²	No./mm	mm		
1×1.5 mm	7/0.52	0.7	16	11
1×2.5 mm	7/0.67	0.8	22	15
1×4.5 mm	7/0.91	0.8	32	21
1×6.0 mm	7/1.04	0.8	38	25
1×7.0 mm	7/1.12	1.0	42	27
1×9.5 mm	7/1.32	1.0	50	32
1×10 mm	7/1.35	1.0	52	34


Fig for Q 5 (ii)

EEE 373

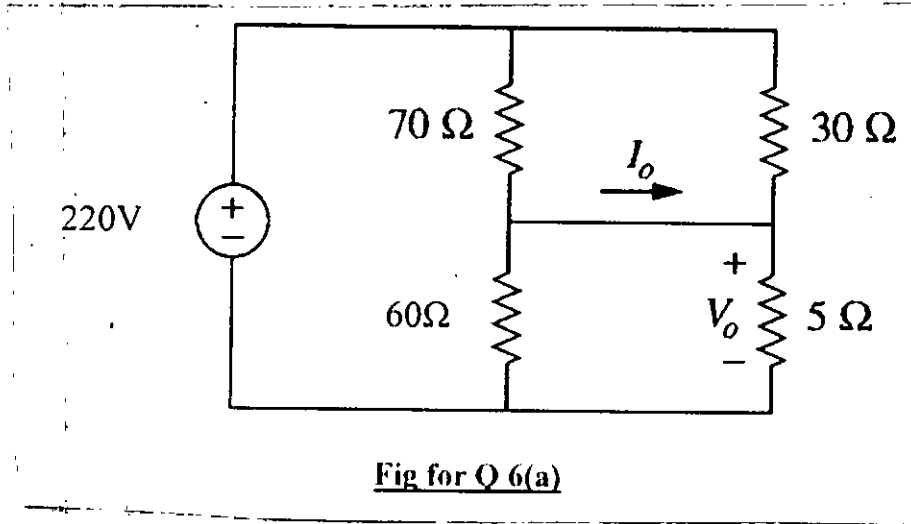
6. (a) For the given circuit, in Fig. for Q 6(a), find the value of current I_0 and Voltage V_0 . (13)



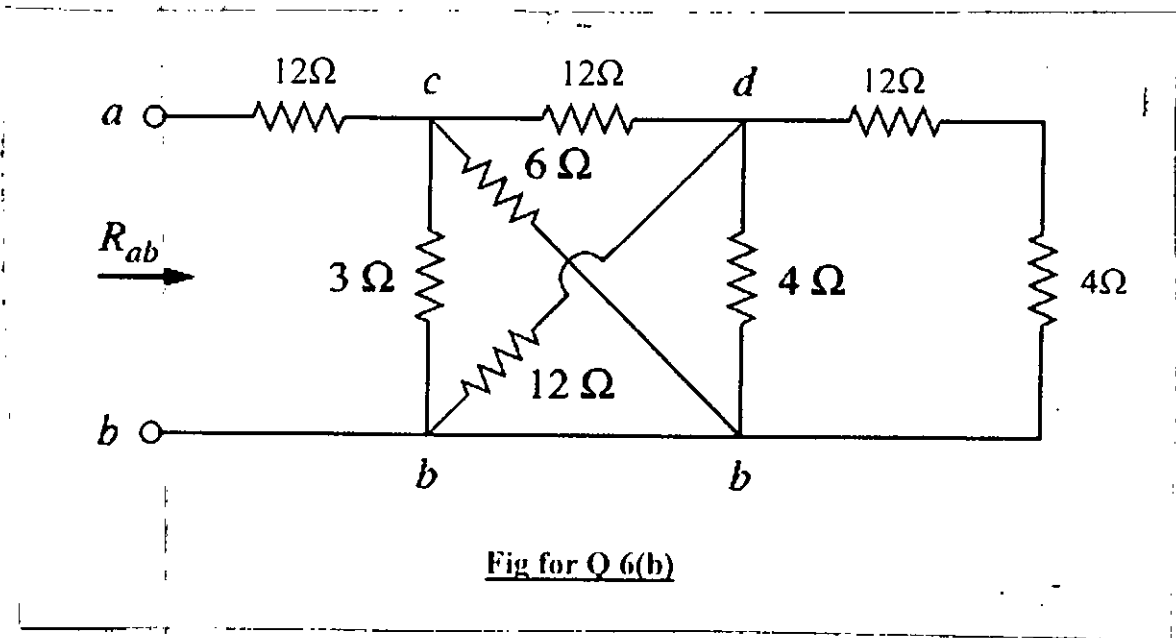- (b) Find the equivalent resistance, R_{ab} for the given network in Fig for Q 6(b). (10)



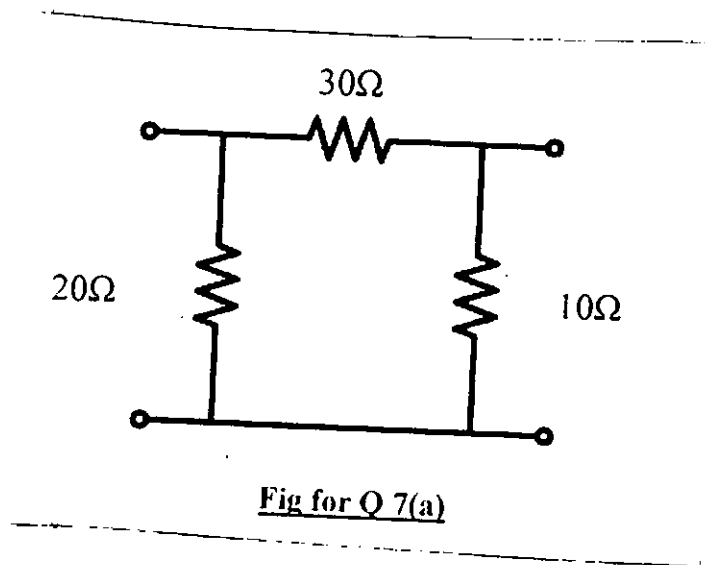7. (a) Convert the given Delta network shown in Fig for Q 7(a) into an equivalent Y network. (12)



(b) For the circuit shown in Fig. for Q 7(b), find the current through each of the resistors using any appropriate network analysis method. (10)

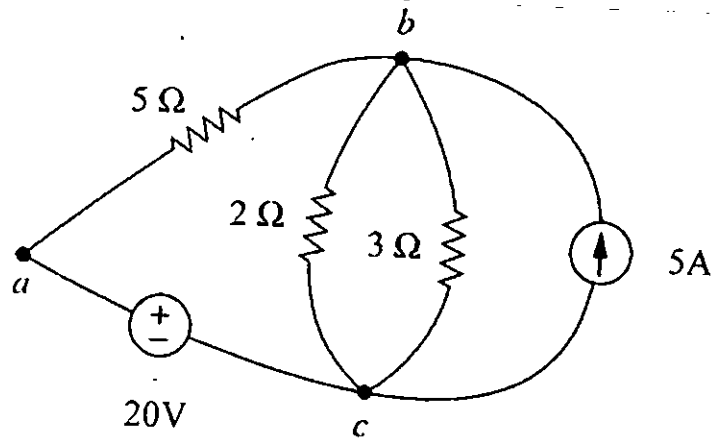


Fig for Q 7(b)

8. (a) The network shown in Fig for Q 8(a) is connected to a current source, $I_{ab} = 16A$. Calculate the voltage across the current source. (13)

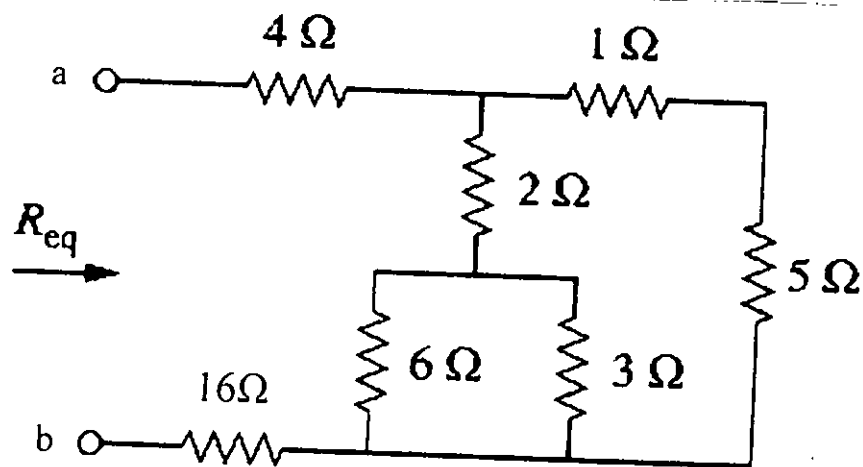


Fig for Q 8(a)

EEE 373

Contd... Q. No. 8(a)

(b) For the circuit shown in Fig for Q 8(a) if a voltage source of 5V voltage and 10Ω series resistance is connected to node a and b, what will be the dissipated power of the 10Ω resistor?

(10)

Course Outcomes of EEE 373

CO No.	CO Statement
1	explain the basic laws of electrical DC and AC circuits, fundamentals of lighting technologies and their applications.
2	apply the knowledge gained to solve DC and AC circuit problems.
3	design electrical wiring system for residential and commercial buildings.